

North South University

Department of Electrical & Computer Engineering

Lab Report

Experiment No: 5

Experiment Title: Design of a Register File

Course Code: CSE332L

Course Name: Computer Organization & Architecture Lab

Name & ID: Md. Rifat Ahmed ~ 1931725042

Date of Experiment: 30/11/2021

Date of Submission: 30/11/2021

1 Objectives:

*Our objective in this experiment is to study how a register title works and a build a register title that has 16 registers.

1 Equipments:

* Logisim Tool

1 Block Dingram:

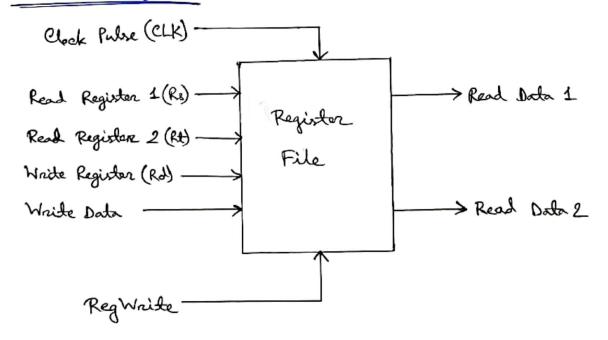


Table:

We'll be building a Register file for the 16-bit ISA with following fields where the formats of the instruction are:

R-type:

OP (4-bit)

OP (4-bit)	Rs (4-bit)	Rt (4-bit)	Rd (4-bit)
I-type:			
OP (4-bit)	Rs (4-bit)	Rt (4-bit)	Immediate (4-bit)
J-type:			

Target (12-bit)

Circuit Diagram:

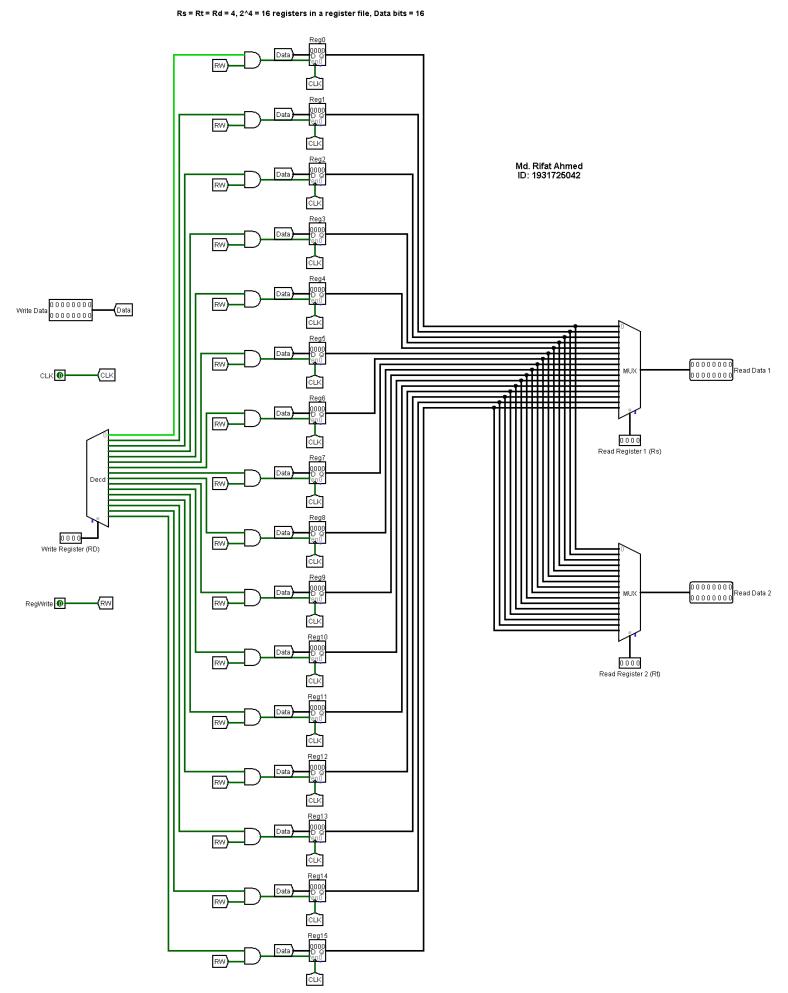


Figure - 2: Circuit diagram of a 4-bit by 4-bit Binary Multiplication Unit

Discussion!

In this experiment we learned how to a register tile works and we also built a register bile with 16 register where all of them are of 16-bits. To construct the circuit in logisim at hirst we took 16 negisters then added the 'write data' in all of the inputs. Then born selecting when to work with which register we used a decoder for Write Register and added it in an AND gate with the 'Reg Write' so that we can control it it should write on not. The registers work work it we set Regwrite to O. Then we added clock pulse, the same one to all the registers and used MUX to get the result know the registers. And it's select bit is the -'Read Register 1', Rs. Then we added another MUX with the results to get 'Read Data 2' and the select bits of this MUX is the 'Read Register 2', Rt. And thus we get a complete Register File that has 16 registers of 16-lits.